
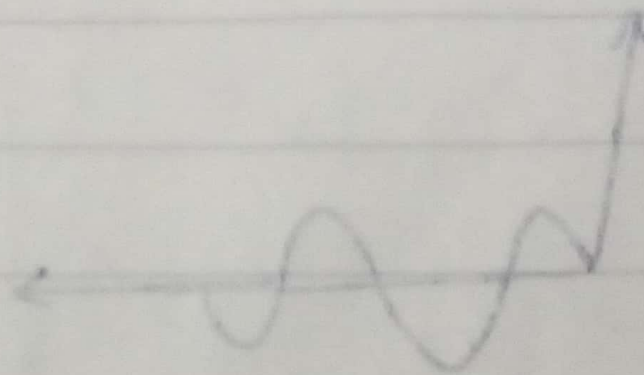


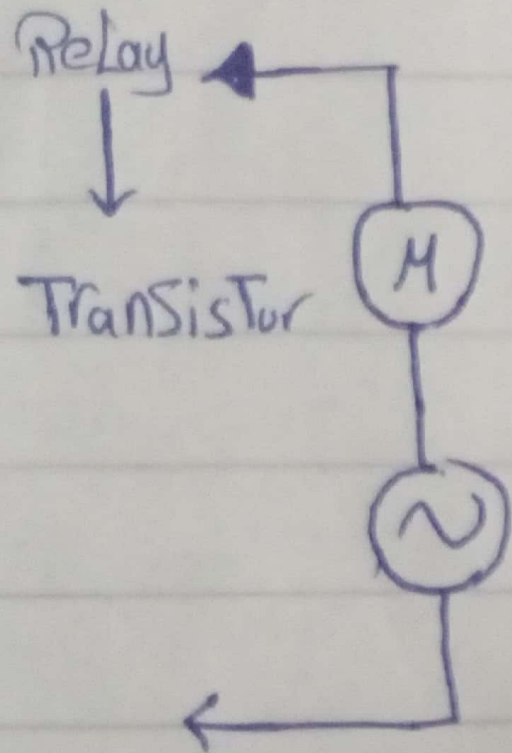using Transistor To Control high voltage devices



Example

→ Transistor used To control relay Consuming 25mA , and $V_{in} = 5V$

$$R_B = ? , \beta = 100,$$

$$I_C = \beta \times I_B = 25 \times 100 = 2500 \times 10^{-3} = 2.5 \times 10^{-3} \times 100 = 0.25 \text{ mA}$$

$$I_B = \frac{25}{100} = 0.25 \text{ mA} \rightarrow 5 \times 0.25 = 1.25$$


$$R_B = \frac{V_{in} - V_{BE}}{I_B} = \frac{5 - 0.7}{1.25} = 3.44 \text{ K}\Omega$$

(1.25 mA) → As when Transistor act as Switch so I_B must be greater than its value by 5 or 10 Times.

* A diode must be used To protect the transistor.



Transistor as ~~multipier~~ (تکثیر) Amplifier

* Works in active region.

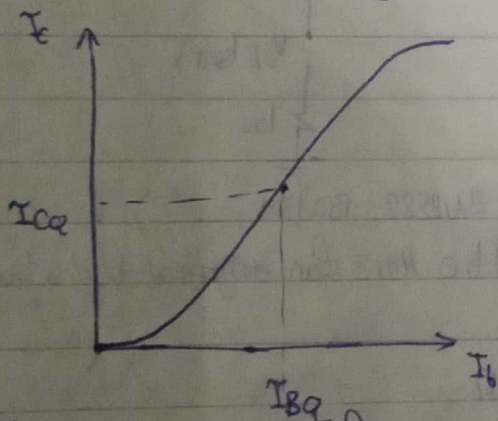


(Q. Point) is Point in which Transistor work.

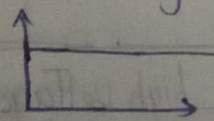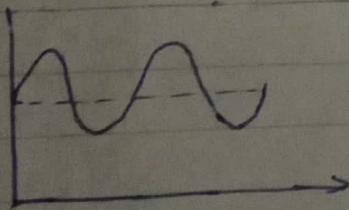* (Bias) → Keep the wave in the active region



DC volt. (Q-Point).

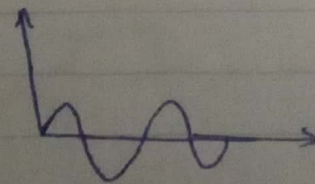

AC

$$* V_{CEQ} = \frac{V_{CC}}{2}$$

Steps To design Transistor as ~~amplifier~~ ~~(common emitter)~~


خطوات

- V_{CE} الجهد
- I_{CQ} التيار
- I_{BQ} التيار
- Bias الجهد

$$V_{CEQ} = \frac{V_{CC}}{2}$$

$$I_{CQ} = \frac{V_{CC} - V_{CEQ}}{R_C}$$

$$I_{BQ} = \frac{I_{CQ}}{\beta}$$

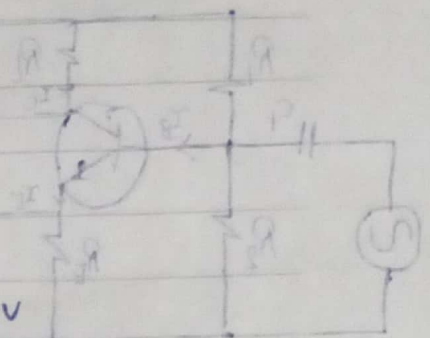

Example.


$$V_{CEQ} = \frac{5}{2} = 2.5V$$

$$I_{CQ} = \frac{5 - 2.5}{1000} = 2.5mA$$

$$\beta = 200 \rightarrow I_{BQ} = \frac{I_{CQ}}{\beta} = 12.5\mu A$$

$$V_{BQ} = 20 \times I_{BQ} + 0.7$$


$$= 0.9V$$

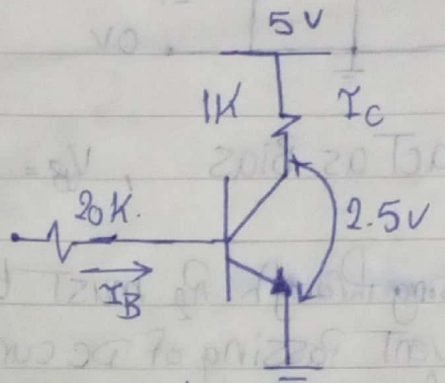

(Gain) كيف تضاعف الإشارة

$$\text{Voltage gain} = \frac{\text{Output}}{\text{Input}} = \frac{V_{out}}{V_{in}}$$


Collector

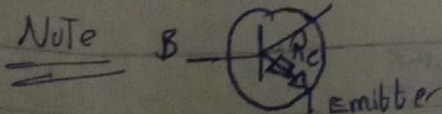

$$R_E = \frac{25}{I_E}$$

$$\text{Gain} = \frac{R_L}{R_E}$$

Example: Common Emitter

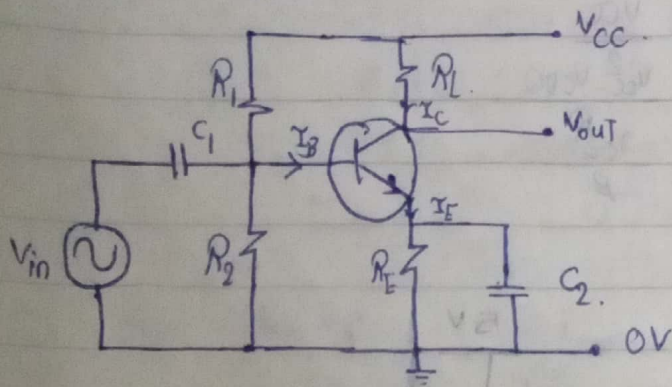

* $(R_1, R_2) \rightarrow$ act as Bias, $V_B = \frac{V_{CC} R_2}{R_1 + R_2}$

* Current passing through R_2 must be 10 times value of I_B

* (C_1) To prevent passing of DC current from V_{CC} and allow the passing of AC current.





$$C_1 > \frac{1}{1000 \pi F}$$

* R_E is used to protect the Transistor from high current and high temperature.

* one of disadvantage of (R_E) that it reduce the value of (Multiply) of the signal, $R_E = 10\% \text{ of } V_{CC}$, $V_E = V_{Bias} - 0.7$.



* $(C_2) \rightarrow$ Avoids the previous disadvantage, $C_2 > \frac{10}{2\pi F R_E}$

Input and output impedance

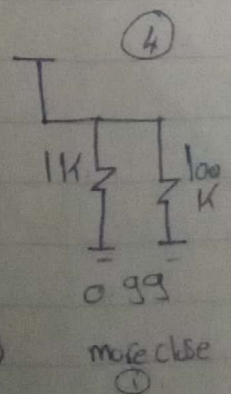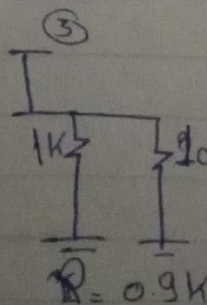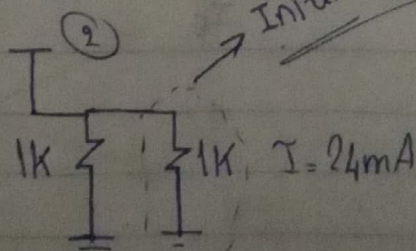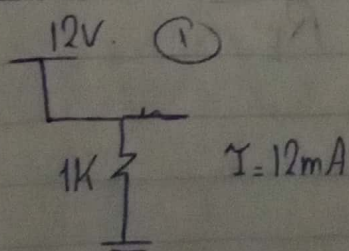

close to ①


For Example.

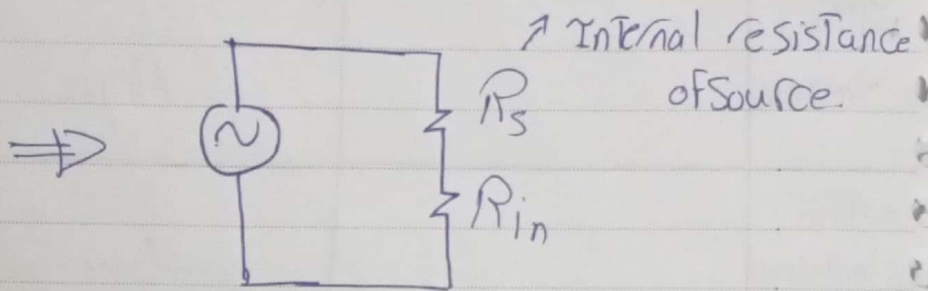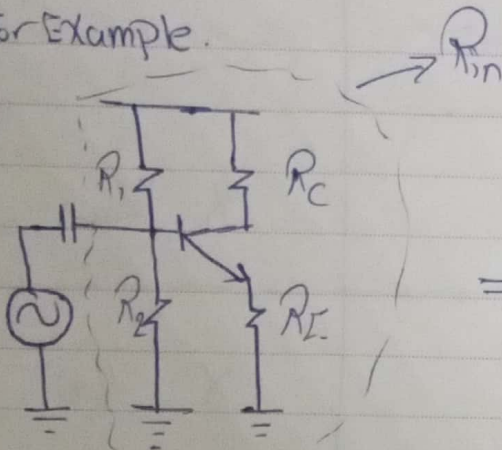




(R_{in} must be larger than R_S) ~~total~~

Note

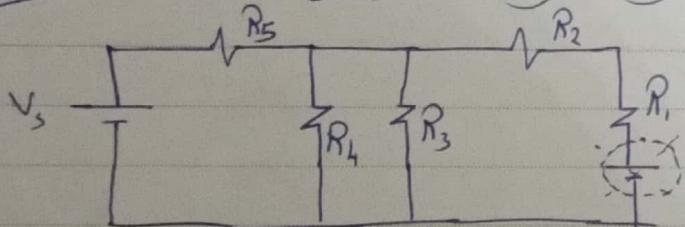يقتصر على مصدر الجهد في الأثر المتكرر من طرف المقاومة



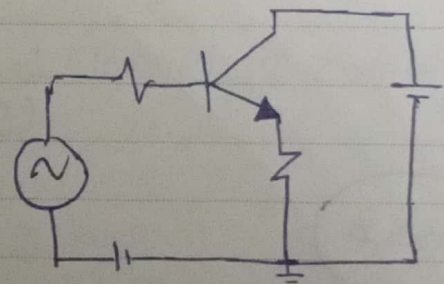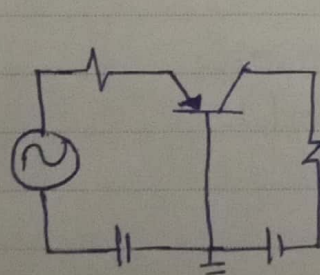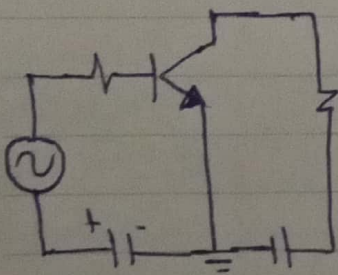Amplifier Connections (Common emitter, Common collector, Common base)



Common emitter

→ Output (opposite input), Phase shift = 180°

→ Amplitude is Amplified

Common base

~~without shifting~~
~~Same Amplitude~~
~~input Resistance very high~~

No shifting
Amplitude is

Amplified
- Not commonly used

Common collector

without shifting
Same Amplitude
input Resistance very high

	Common Emitter	Common Collector	Common base
input internal Impedance		High	X Low
output impedance		Low	X High
Amplifier	✓	Same	✓ (Not Used)

~~* We can design by using Application Transi~~


* Amplifier classes :

class A

$$P = VI \neq 0$$

- Q-Point at middle.

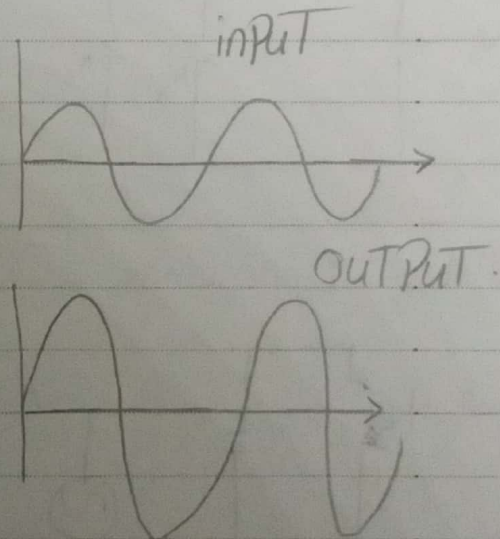- Consumes DC current, low efficiency (25-30%)




class B

$$P = VI = 0$$


- Q-Point near to cutoff region

- Consumes current only when signal is available

- High efficiency (70-80%)

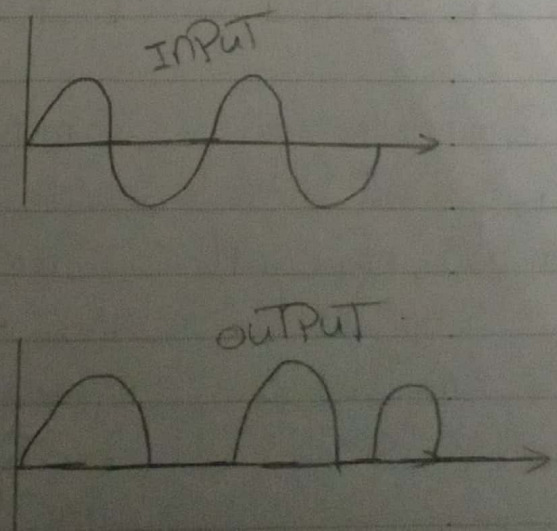


class AB

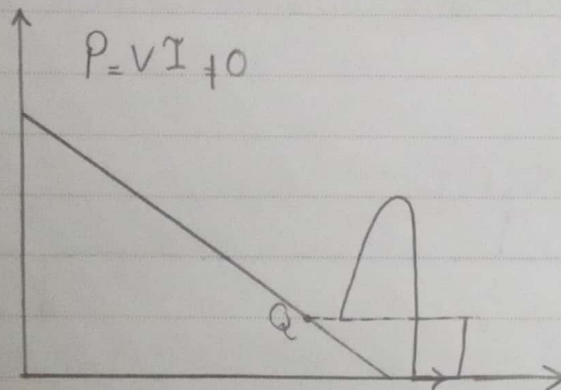


- Q-Point between cutOff region and middle.
- efficiency is High. (Better than A, Less than B)

class c Not used as Amplifier.

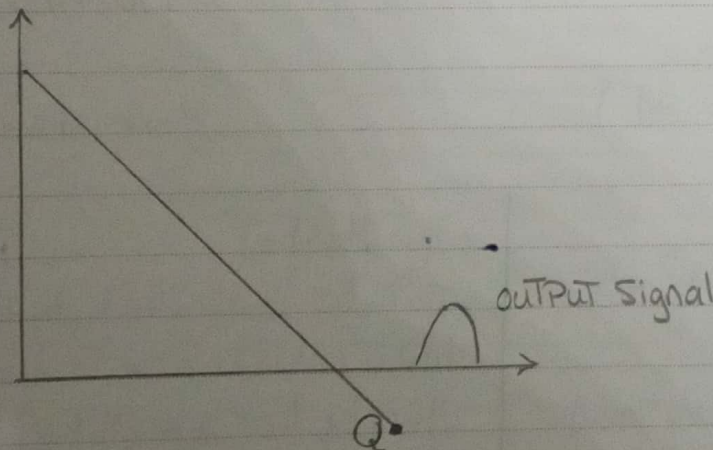

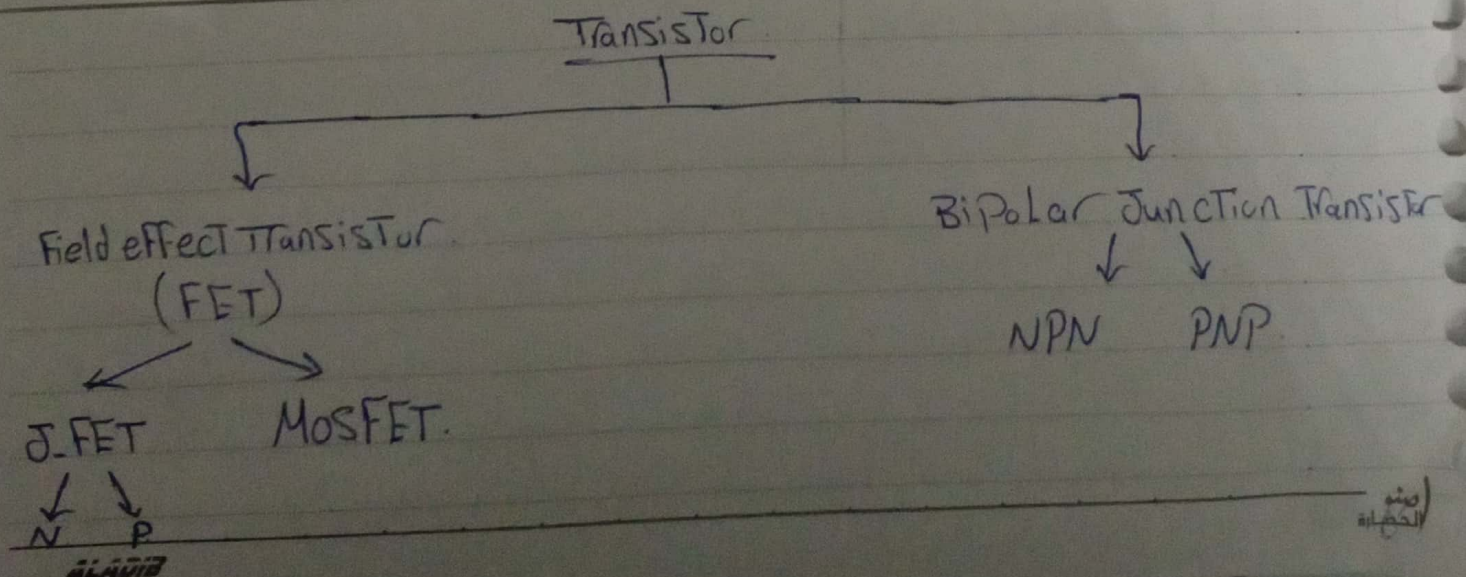- Q Point is out cutOff region.
- efficiency is Very high, (Higher than 80)




in case of (MOSFET) → doesn't consume current to control, so the input resistance is very high

MOSFET

Depletion (N, P)

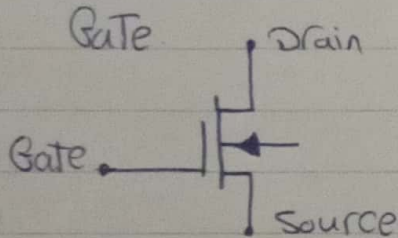Transistor (is on) without any ~~potential~~ voltage on Gate



(Normally opened.)

Enhancement (N, P)

opposite to Depletion

(Normally closed)

More used

→ BJT


- Can be controlled by the current on base
- input resistance very small
- ability to ~~control~~ Amplify current is Low

~~etc~~
- Percentage to be damaged is very Small

→ MOSFET


- Can be controlled by ^{Potential difference} ~~voltage~~ on the gate
- input resistance is very high
- Ability to Amplify current is high
- Percentage of damage is very high
- Works on high frequencies

(MOSFET) as a Switch

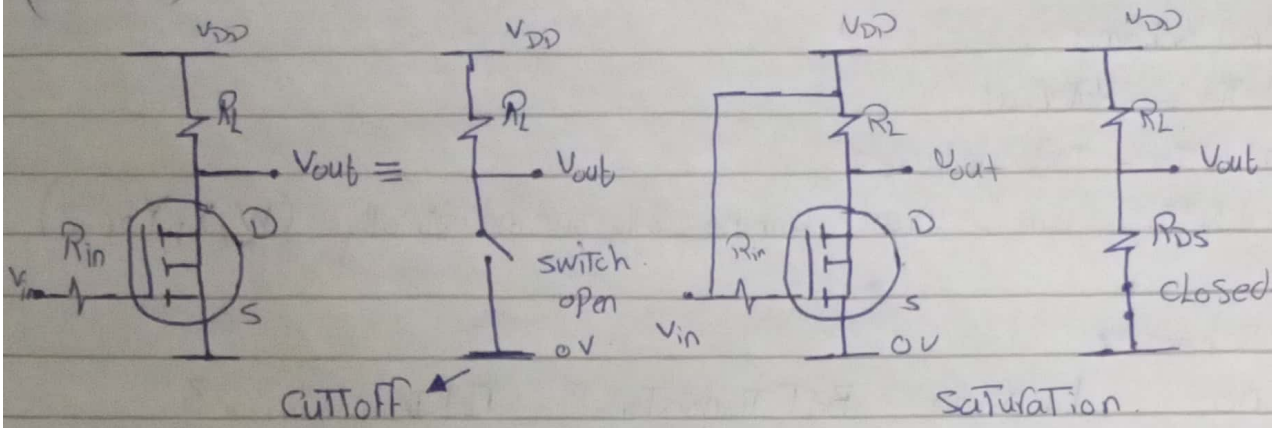


→ We should choose (MOSFET) with small R_{DS} To Minimize Power dissipation.

How to examine Transistor (BJT)?

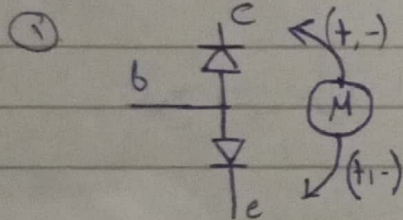


إذا أعطى قراءة لا خير فهو تالف

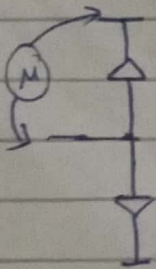

Forward - يجب أن نصل على قراءة مقاومة بين (500.1k)
Reverse - " أن نصل على مقاومة عالية

② By using digital Multimeter, (diode) function, we should get a value between 0.3-0.8V.

How To examine Transistor MOSFET?

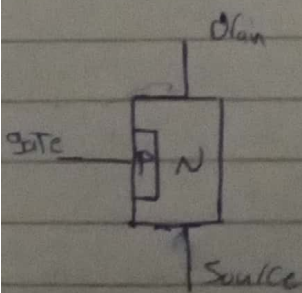

- 1) By using digital Multimeter on (diode) function or Resistance.
- 2) Connect or let the Gate To Touch Source
- 3) (-ve) Connect To Source
- 4) (+ve) Connect To drain
- 5) then put the (+ve) probe on the Gate
- 6) Finally touch gate and source, the value will be very high.

Transistor Coding

① Pro. election scheme

- First Letter = Material
- Second Letter = Type and uses
- Third Letter = Can be used: Commercially and industrially (W, X, Y or Z)

② JEDEC Scheme


- First no: 1 = Diode, BJT Transistor = 2, FET Transistor = 3.
- Second Letter N
- Third Letter (رقم 3)

(IGBT) Transistor

BJT

FET


يجمع بين مزايا BJT و FET

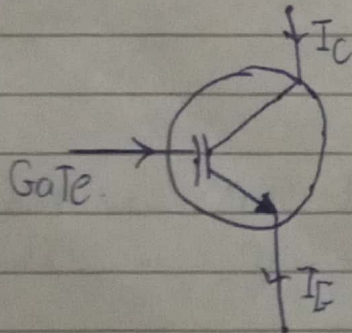

- Doesn't consume current.
- Can be controlled by potential.
- High ability to withstand current.
- the most expensive.

Applications → inverters, (محركات 3 phase), Power supply.

Thyristor

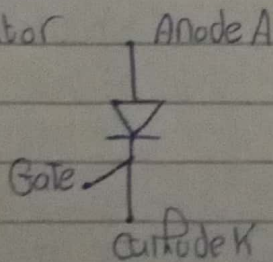


(Its function like the Diode but it differs, that it must be given a pulse on its gate to pass current from Anode to Cathode)

- we can control the ~~gate~~ thyristor through gate
- if we give the gate any voltage, the thyristor will be on and act as a diode
- if we remove the voltage on gate, the thyristor remains on without any change
- we can change it to (OFF) if the voltage on Anode becomes (-ve) or removing the source, or by making short circuit between Anode and Cathode
- if the current passing through thyristor reaches "minimum holding current"
 # thyristor will be OFF

Diac: Element which is similar to diode

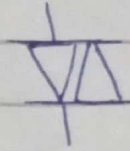- it needs more voltage to pass the current.
(Breakdown voltage) V_{BR}



has no (anode and cathode)

* How to Examine diac.


By using DMM to the Poles of Diac and change the Poles ~~are~~ to take the readings in both cases and they must be equal

Triac: it is similar to the thyristor but it can pass current in both directions

Applications → used to control loads working on AC currents

Disadvantage of Triac

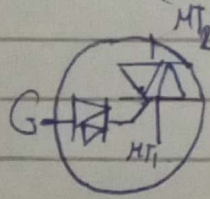
- ~~Signal~~ +ve signal on the gate to open may be not equal to the (-ve)
- So, to solve this problem we use a diac to avoid this problem.
- Also there is another element called (Quadriac) which consists of a diac and a triac together.




→ How to examine Triac?

Put Positive Probe on the Gate and MT1 and the negative Probe on MT2, so the Resistance will be very small value.

Voltage Regulator

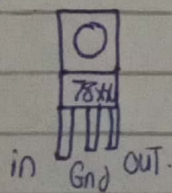

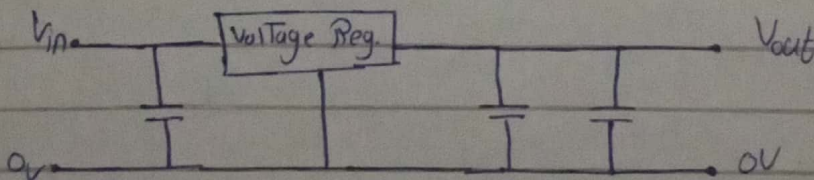(xx) → identify the input and output voltage



(Voltage Regulators), decreases its Temperature at certain point to protect itself from ~~damaging~~ damaging